

## Register File

To simulate Register file which has collection of 32 registers. The size of each register is 64 bits wide. Also, we have to support R type ALU Instruction. A register file is an array of processor registers in a central processing unit (CPU). Below are the steps involved:

- a. Design register file using register address inputs rd\_addr\_1 , rd\_addr\_2 and wr\_addr 5 which are 5 bit wide, data input 64 bits wide and input control input. It will store the values in 32 register.
  - b. Design combine RF with ALU. Where ALU read data from register file and perform operation on it.
  - c. Design write back logic which will store the ALU result back to register file.
- Simulation of register file

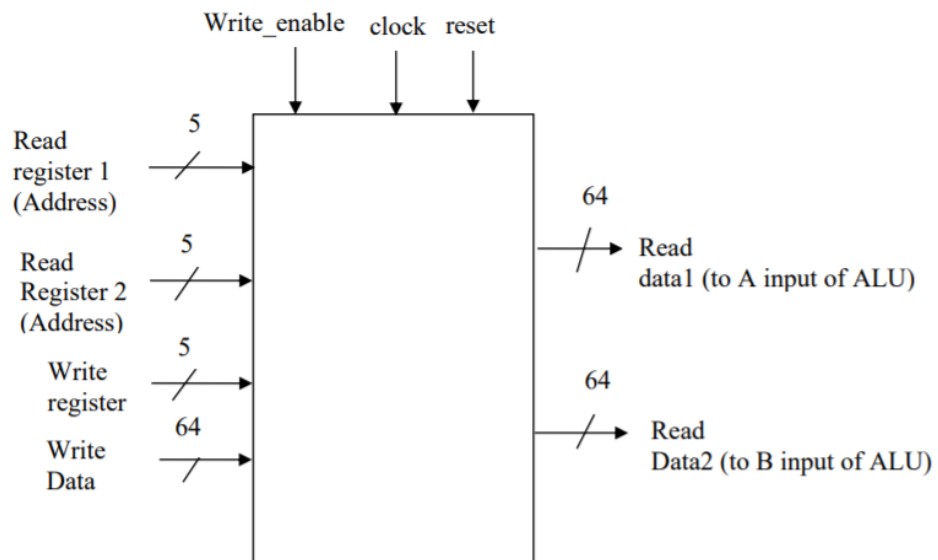


Figure 1. Register File


Register file operation parameters are:

- Input clk, reset, wr\_en 1 bit
- Input rd\_addr\_1, rd\_addr\_2, wr\_addr 5 bit
- Input d\_in 64 bit
- Output d\_out\_1, d\_out\_2 64 bit

Module Name: regfile

Test Module Name: regfile\_tb

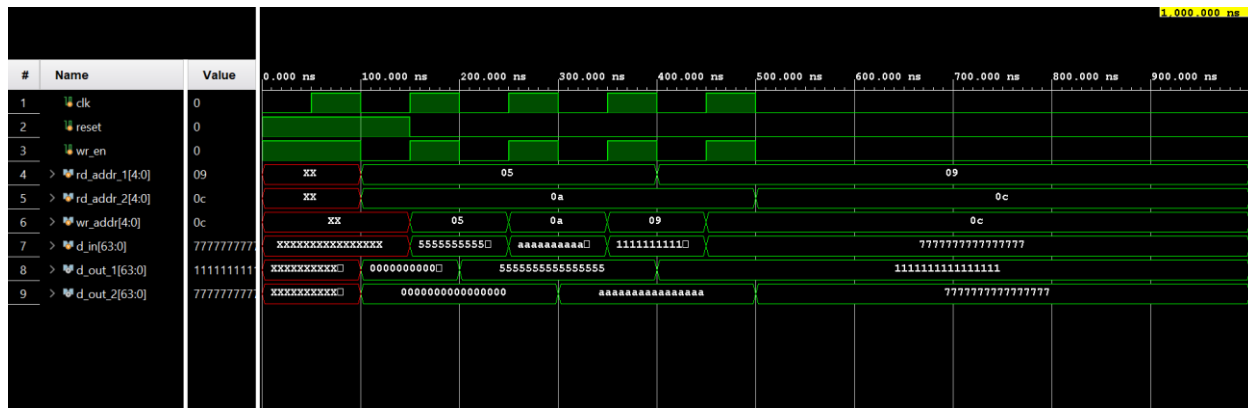Below screen shot show the waveform for input and output parameters of Register file.



Here we are creating register file of 53 registers hence the address inputs are 5 bits. First, we are resting the register file by enabling the reset signal. We are setting rd\_addr\_1 to 5 and rd\_addr\_2 to 10. Then we are writing 64'h5555555555555555 to register 5 on positive edge and 64'haaaaaaaaaaaaaaaa to register 10 on next positive edge. In the testbench we are first setting the value of register address with data input and the changing the clk value so that correct data will be store in the register. And correct data will be read on next clock edge.

- Simulation of register file with ALU

 


Figure 2. Register File feeding ALU

Register file with ALU operation parameters are:

- input ALUOp 2 bits
- input Opcode\_field 11 bits
- input clk 1 bit
- input reset 1 bit
- input wr\_en 1 bit
- input rd\_addr\_1, rd\_addr\_2, wr\_addr 5 bits
- input d\_in 64 bits
- output ALU\_result 64 bits
- output Zero 1 bit

Module Name: RFwithALU


Test Module Name: RFwithALU\_tb

Below screen shot show the waveform for input and output parameters of Register file with ALU.



Here we consider register 5,10 as A, B and assign value 64'h5555555555555555, 64'haaaaaaaaaaaaaaaaaa respectively. The output of register file is the input to ALU unit. Based on opcode and ALU opcode value we perform ALU operation on the data stored in register 5 and 10.

- Simulation of Write back.

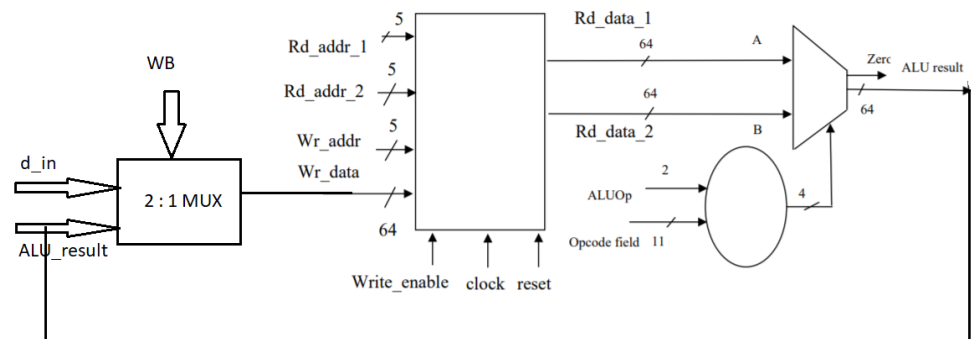


Register file with ALU and write back operation parameters are:

- input ALUOp 2 bits
- input Opcode\_field 11 bits
- input clk 1 bit
- input reset 1 bit
- input wr\_en 1 bit
- input rd\_addr\_1, rd\_addr\_2, wr\_addr 5 bits
- input d\_in 64 bits
- output ALU\_result 64 bits
- output Zero 1 bit
- input WB 1 bit

Module Name: RFwithALUandWB

Test Module Name: RFwithALUandWB\_tb

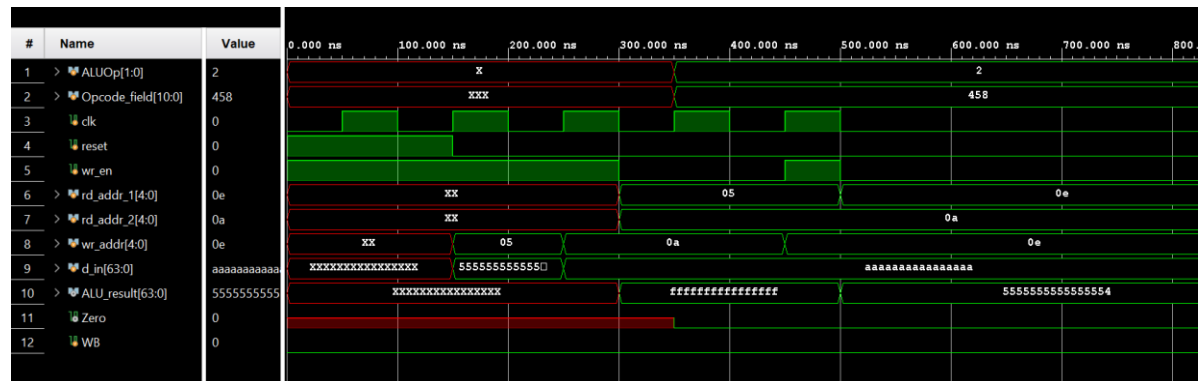Below screen shot show the waveform for input and output parameters of Register file with ALU and write back.



Here we have introduced one input called write back. If the this signal is set the module is loading the value at ALU\_result output to the write register specified by wr\_addr. This implementation is simulation R-type instruction. In the teste bench we are simulation below instruction :

ADD X1, X2, X3

Where, 5 and 10 are source register and 12 is the destination register.